

# CU Design Document

Martin Mueller & Isaiah Ley

Due: 11/17/2020 8:00 A.M.

The control unit takes as input the contents of the  $C$  register, the least significant bit of  $Q$  ( $Q_0$ ), and the value of the 1 bit register  $Q_{-1}$  and outputs  $C - 1$  as well as two control bits: one specifying if an arithmetic operation needs to be performed on the accumulator register (*math*) and one specifying if that operation must be subtraction (*sub*). Below is the truth table for the CU. Since the output of  $C$  is always  $C - 1$ , it has been left out.

$Q_0$	$Q_{-1}$	$math$	$sub$
0	0	0	0
0	1	1	0
1	0	1	1
1	1	0	0